

模拟与数字电路

Analog and Digital Circuits



课程主页 扫一扫

第五讲：基于卡诺图的化简，组合逻辑


Lecture 5: K-map Logic Simplification

主讲：陈迟晓

Instructor: Chixiao Chen

提纲

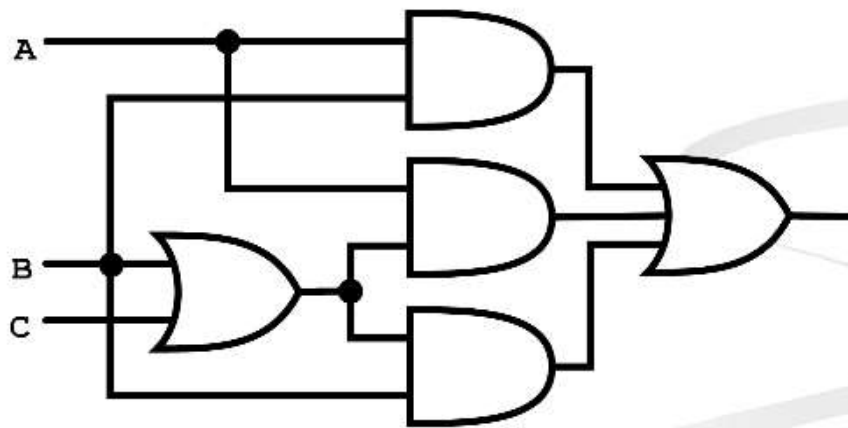- 复习
 - 写出右图的逻辑表达式
 - 对该表达式化简
 - 译码器和编码器的区别?
- 卡诺图
- 基于卡诺图的化简
- 组合逻辑
- 基于级联思想的复杂逻辑实现



从真值表到卡诺图

	W	X	Y	Z	F_{WXYZ}
Minterm - 0	0	0	0	0	0
Minterm - 1	0	0	0	1	1
Minterm - 2	0	0	1	0	1
Minterm - 3	0	0	1	1	0
Minterm - 4	0	1	0	0	1
Minterm - 5	0	1	0	1	1
Minterm - 6	0	1	1	0	0
Minterm - 7	0	1	1	1	1
Minterm - 8	1	0	0	0	0
Minterm - 9	1	0	0	1	0
Minterm - 10	1	0	1	0	1
Minterm - 11	1	0	1	1	0
Minterm - 12	1	1	0	0	1
Minterm - 13	1	1	0	1	0
Minterm - 14	1	1	1	0	1
Minterm - 15	1	1	1	1	1

Four Variable K-Map

	$\bar{Y}\bar{Z}$	$\bar{Y}Z$	YZ	$Y\bar{Z}$
$\bar{W}\bar{X}$	0 ₀	1 ₁	0 ₃	1 ₂
$\bar{W}X$	1 ₄	1 ₅	1 ₇	0 ₆
$W X$	1 ₁₂	0 ₁₃	1 ₁₅	1 ₁₄
$W\bar{X}$	0 ₈	0 ₉	0 ₁₁	1 ₁₀

- 最小项:包含全部变量的乘积项, 且变量仅出现一次


- 卡诺图:将n 变量的全部最小项各用一个小方块表示, 并使具有逻辑相邻性的最小项在几何位置上也相邻地排列起来, 所得图形叫做卡诺图

从SOP表达式到卡诺图

- 乘积项值为1，则在卡诺图对应位置填1

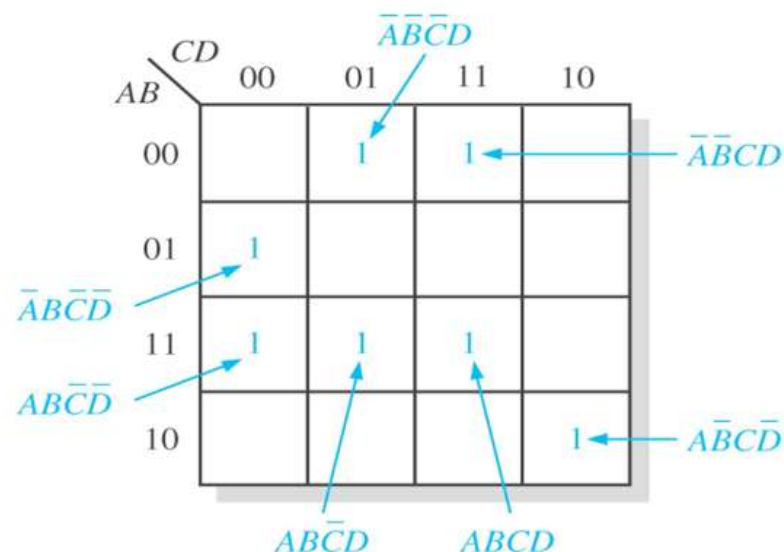- 例题

$$\bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + AB\bar{C}D + ABCD + AB\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + A\bar{B}C\bar{D}$$



- 注意此处表达式为标准SOP格式

从SOP表达式到卡诺图

- 非标准SOP表达式 => 卡诺图

- 例题 $\bar{A} + A\bar{B} + AB\bar{C}$

乘积项扩展


\bar{A}	$A\bar{B}$	$AB\bar{C}$
$\bar{A}BC=011$	$A\bar{B}C=101$	$AB\bar{C}=110$
$\bar{A}B\bar{C}=010$	$A\bar{B}\bar{C}=100$	
$\bar{A}\bar{B}C=001$		
$\bar{A}\bar{B}\bar{C}=000$		

填入卡诺图


AB \ C	0	1
00	1	1
01	1	1
11	1	
10	1	1

卡诺图化简


- 例子

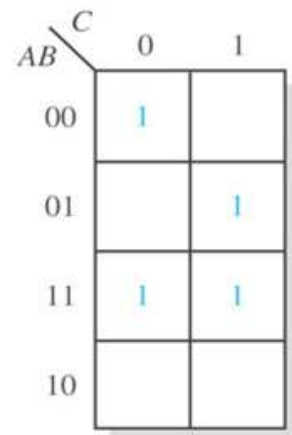


(a)

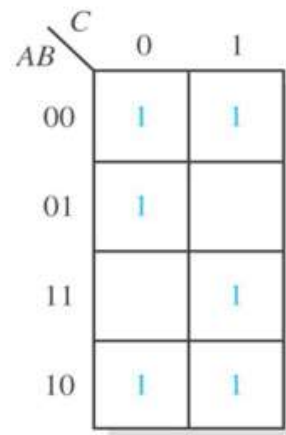


(b)

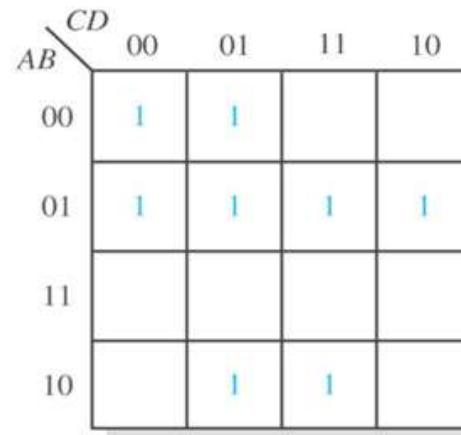


(c)

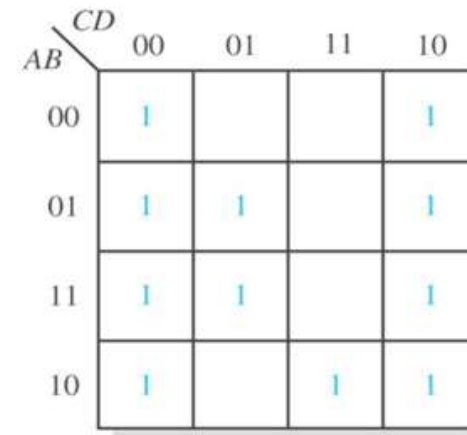


(d)

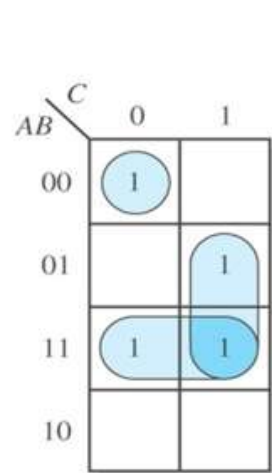


(a)

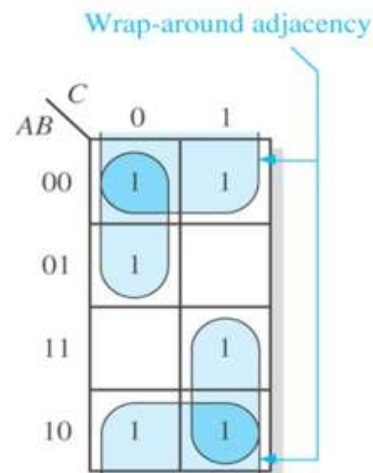

(b)

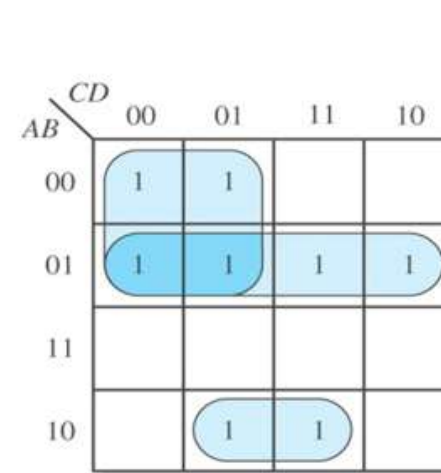


(c)

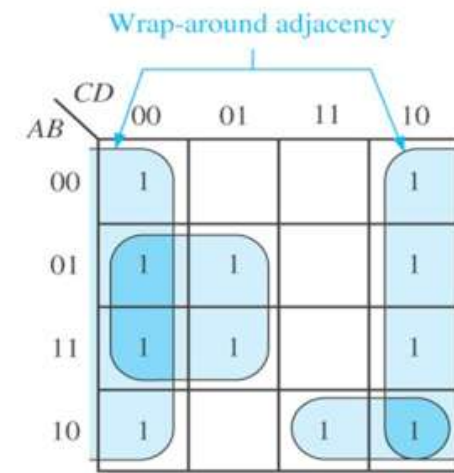

(d)

卡诺图化简

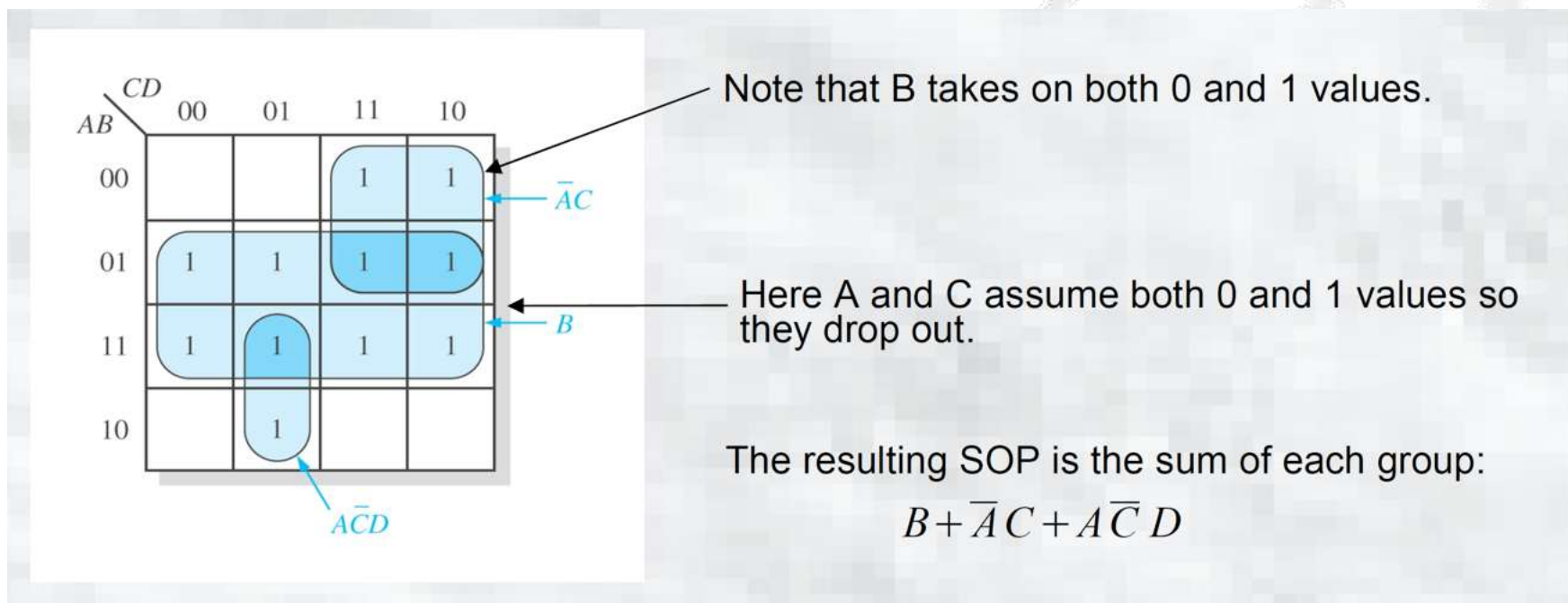- 如何得到最简SOP表达式
 - 圈出 1 之后，找出圈内没有改变的变量并保留
 - 一组必须包含1,2,4,8,16...个 1
 - 例: 将如下卡诺图化简为最简SOP表达式




卡诺图化简

- 直接由真值表化简

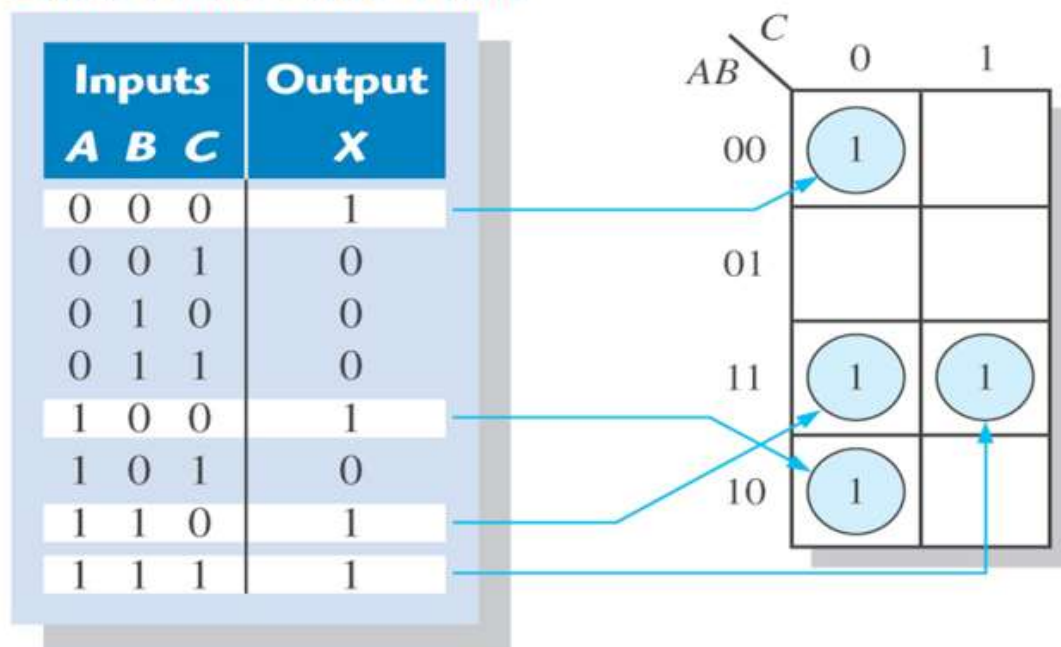- 例:

$$X = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$



- Don't care 情形

- 有时某种变量组合不被允许。这种情况下在卡诺图和真值表中用“X”表示

卡诺图化简

(1) 任何2个标1的相邻最小项，可以合并为一项，并消去1个变量（消去互为反变量的因子，保留公因子）

BC		00	01	11	10	
A						
0	1	0	0	0	1	$\bar{A}\bar{B}\bar{C}$ + $\bar{A}BC$ = $\bar{A}\bar{C}(\bar{B} + B)$
1	0	1	1	0	0	

$$\boxed{\cancel{\bar{A}\bar{B}\bar{C}} + \cancel{ABC}} = AC = \bar{A}\bar{C}$$

CD		00	01	11	10	
AB						
00	0	1	0	0		$ABC\bar{D}$ + $ABCD$ = $BC\bar{D}$
01	0	0	0	1		
11	0	0	0	1		
10	0	1	0	0		

$$\cancel{\bar{A}BC\bar{D}} + \cancel{ABCD} = \bar{B}CD$$

卡诺图化简

(2) 任何4个标1的相邻最小项，可以合并为一项，并消去2个变量

BC		00	01	11	10
A	0	1	1	1	1
	1	0	1	1	0

$$\begin{aligned}
 & \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC \\
 &= (\bar{A}\bar{B} + \bar{A}B + \bar{A}\bar{B} + \bar{A}B)C \\
 &= [\bar{A}(\bar{B} + B) + A(\bar{B} + B)]C \\
 &= C
 \end{aligned}$$

$$\begin{aligned}
 & \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC \\
 &= (\bar{B}\bar{C} + \bar{B}C + B\bar{C} + BC)\bar{A} \\
 &= [B(\bar{C} + C) + B(C + \bar{C})]\bar{A} \\
 &= \bar{A}
 \end{aligned}$$


CD		00	01	11	10
AB	00	0	1	0	0
	01	1	1	1	1
	11	0	1	1	0
	10	0	1	0	0

$\bar{A}B$ (points to row 01)
 $\bar{C}D$ (points to column 01)
 BD (points to column 11)


卡诺图化简

(3) 任何8个标1的相邻最小项，可以合并为一项，并消去3个变量

AB \ CD		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0




AB \ CD		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	1	0	0	1
	11	1	0	0	1
	10	1	0	0	1




卡诺图化简

(3) 任何8个标1的相邻最小项，可以合并为一项，并消去3个变量

AB \ CD		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0



AB \ CD		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	1	0	0	1
	11	1	0	0	1
	10	1	0	0	1



卡诺图化简原则

- 卡诺图尽可能圈大，先圈大后圈小
- 每个圈只能含有 2^n 个相邻项。要特别注意对边相邻性和四角相邻性
- 圈的个数尽量少
- 卡诺图中所有取值为1的方格都要被圈过，即不能漏掉取值为1的最小项
- 将每一个圈对应的与项进行逻辑加，即得到与或表达式。

例题

【例1】用卡诺图化简逻辑函数
 $F(A, B, C) = \sum(1, 2, 3, 6, 7)$ 的最简与或表达式。

解: 1. 画出函数F的
三变量卡诺图。

BC \ A	00	01	11	10
0	0	1	3	2
1	4	5	7	6

2. 把函数F表达中出现的最小项，在卡诺图对应小方格中填上1，其余方格填0(常不填)。

$$F(A, B, C) = \sum(1, 2, 3, 6, 7)$$

3. 合并最小项。
圈卡诺圈

BC \ A	00	01	11	10
0	0	1	1	1
1	4	5	1	1

Diagram showing two prime implicants circled: $\bar{A}C$ (orange circle) and B (pink circle).

4. 写与或表达式
 $F(A, B, C) = \sum(1, 2, 3, 6, 7) = \bar{A}C + B$

例题

【例2】用卡诺图化简函数

$$F(A,B,C,D) = \overline{A}\overline{B}CD + A\overline{B}\overline{C}D + AB\overline{C}D + A\overline{B}CD$$

解:根据最小项

的编号规则,可知

$$F = m_3 + m_9 + m_{11} + m_{13}$$


得卡诺图。

$$F = A\overline{C}D + \overline{B}CD$$


AB \ CD	CD			
	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

例题

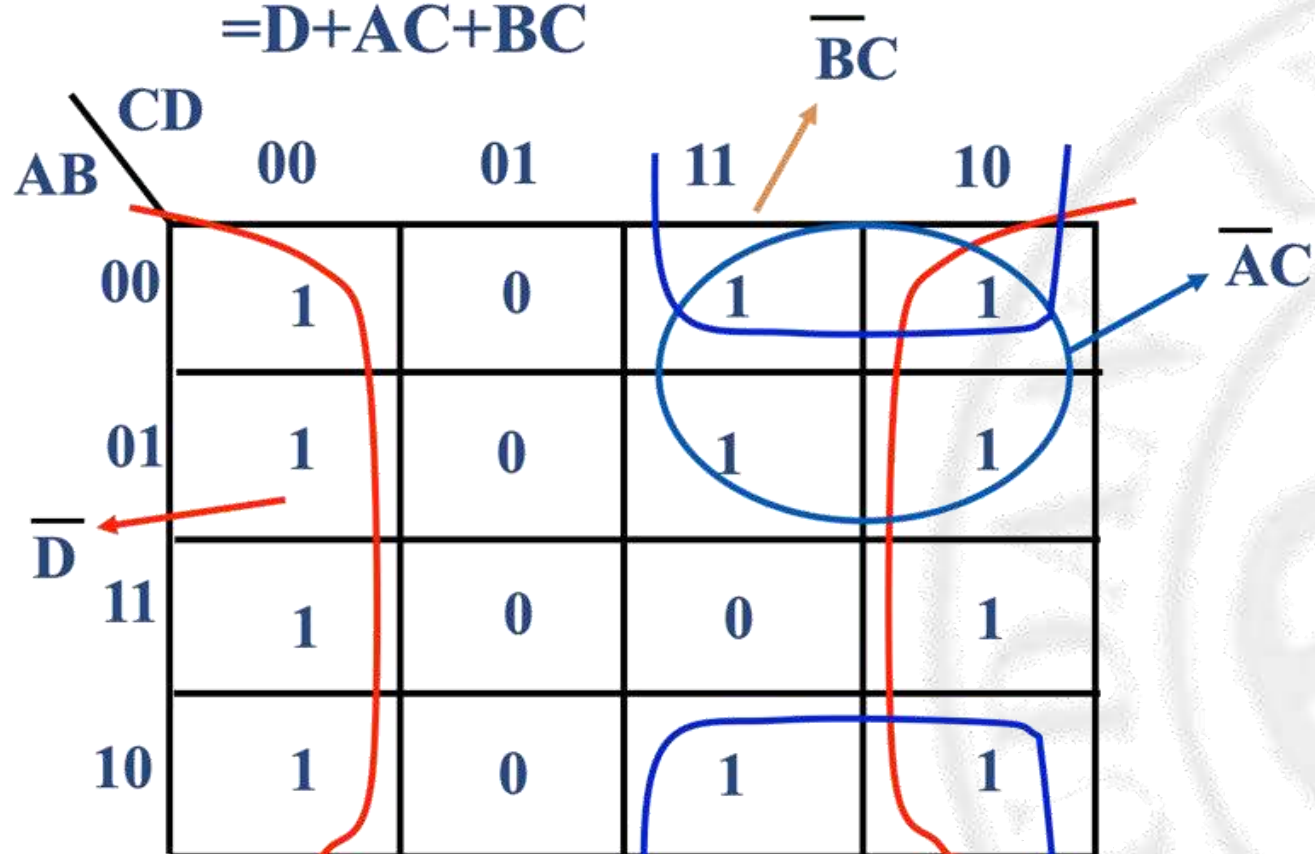例: $Y = AB\bar{D} + \bar{D} + \bar{A}DBC + \bar{A}C + \bar{B}C$
 $= \bar{D} + \bar{A}C + \bar{B}C$



BCD-7段显示译码器

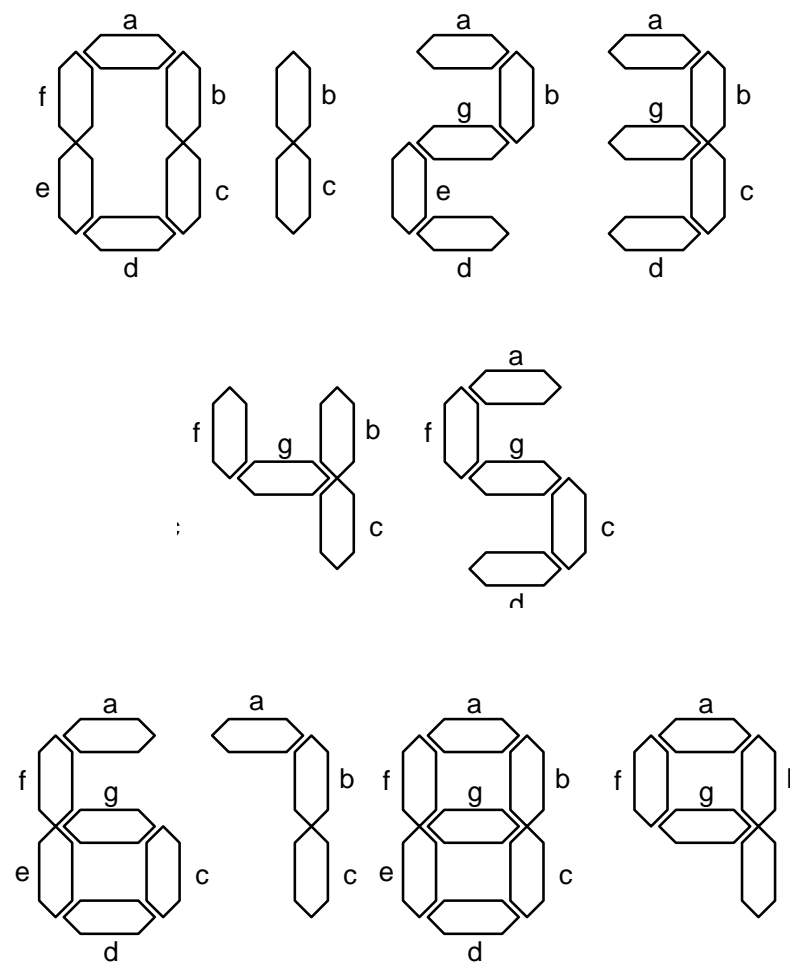

Digit	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	1	1	0	0	1	1	1	1
2	0	0	1	0	0	0	1	0	0	1	0
3	0	0	1	1	0	0	0	0	1	1	0
4	0	1	0	0	1	0	0	1	1	0	0
5	0	1	0	1	0	1	0	0	1	0	0
6	0	1	1	0	0	1	0	0	0	0	0
7	0	1	1	1	0	0	0	1	1	1	1
8	1	0	0	0	0	0	0	0	0	0	0
9	1	0	0	1	0	0	0	0	1	0	0

BCD-7段显示译码器 - 卡诺图化简

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	×	×	×	×
10	1	1	×	×

$$a = A + C + BD + \overline{B}\overline{D}$$

AB \ CD	00	01	11	10
00	1	0	1	1
01	1	0	1	0
11	×	×	×	×
10	1	1	×	×

$$b = \overline{B} + \overline{C}\overline{D} + CD$$

AB \ CD	00	01	11	10
00	1	1	1	0
01	1	1	1	1
11	×	×	×	×
10	1	1	×	×

$$c = B + \overline{C} + D$$

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	0	1
11	×	×	×	×
10	1	1	×	×

$$d = \overline{B}\overline{D} + C\overline{D} + B\overline{C}D + \overline{B}C + A$$

AB \ CD	00	01	11	10
00	1	0	0	1
01	0	0	0	1
11	×	×	×	×
10	1	0	×	×


$$e = \overline{B}\overline{D} + C\overline{D}$$

AB \ CD	00	01	11	10
00	1	0	0	0
01	1	1	0	1
11	×	×	×	×
10	1	1	×	×

$$f = A + \overline{C}\overline{D} + B\overline{C} + B\overline{D}$$


组合逻辑 Combinational Logic

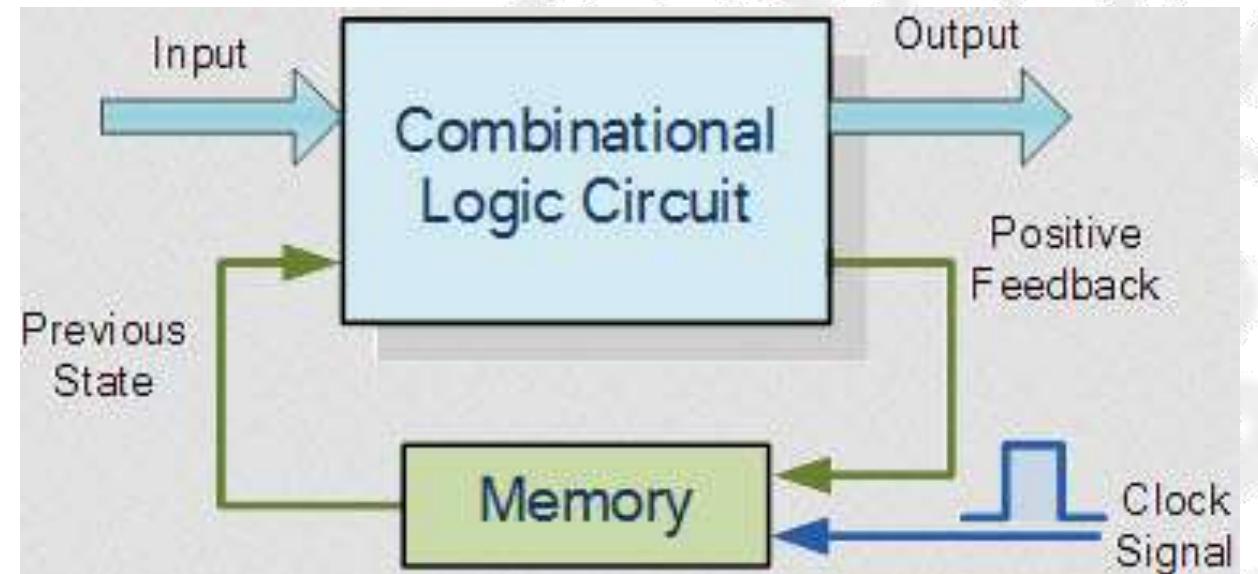- 定义：任一时刻的输出状态只取决于该时刻的输入状态的组合，而与电路的以前状态无关。电路只是由门电路组成，没有记忆单元，也没有反馈电路。




Exclusive-OR Gate


- 真值表

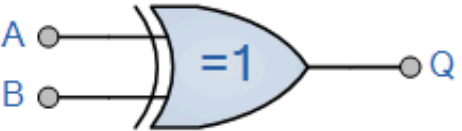Symbol	Truth Table		
 2-input Ex-OR Gate	B	A	Q
	0	0	0
	0	1	1
	1	0	1
	1	1	0
Boolean Expression $Q = A \oplus B$		A OR B but NOT BOTH gives Q	

- 基于SOP/CMOS的表达式

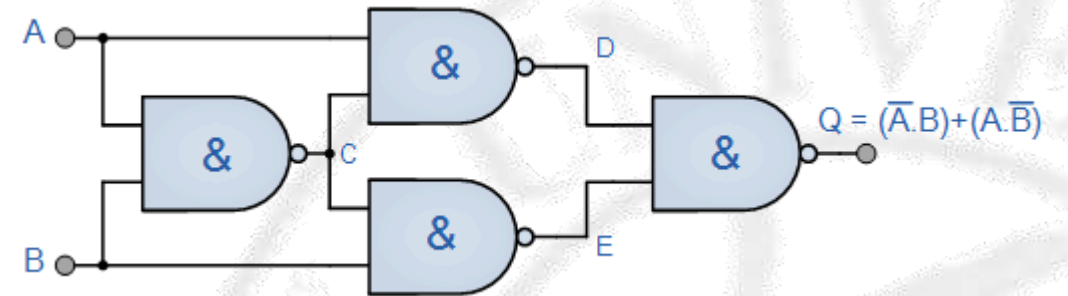


- 非CMOS电路的XOR实现

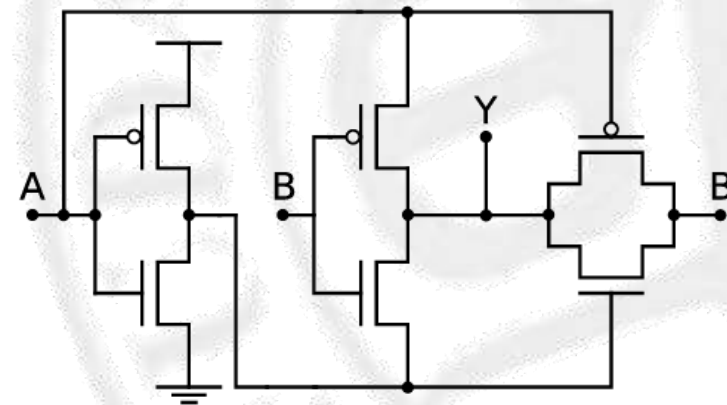

半加器 Half Adder

- 两个1bit 输入， 一个2bit 输入出的无符号加法器

Truth Table			
Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

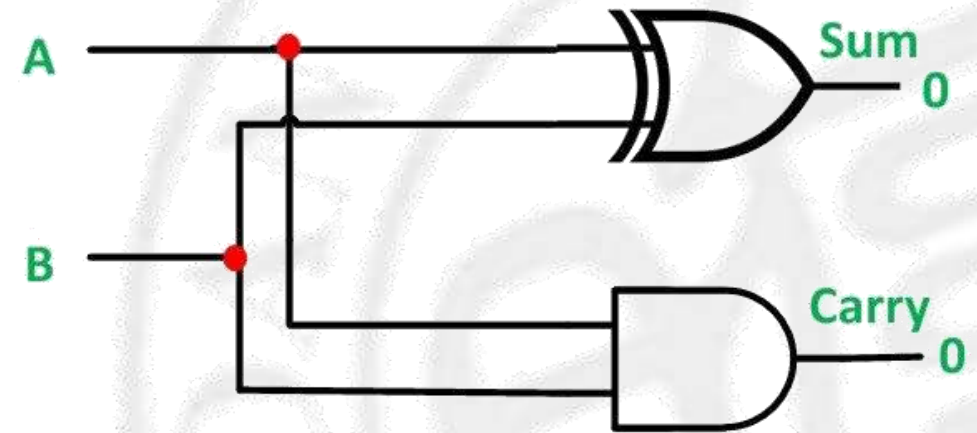

Two Bit Adder (continued)

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	0	1	1	1
10	0	0	1	1

X

AB \ CD	00	01	11	10
00	0	0	1	1
01	0	1	0	1
11	1	0	1	0
10	1	1	0	0

Y

AB \ CD	00	01	11	10
00	0	1	1	0
01	1	0	0	1
11	1	0	0	1
10	0	1	1	0

Z

$$X = AC + BCD + ABD$$

$$Z = BD' + B'D = B \text{ xor } D$$

$$Y = A'B'C + AB'C' + A'BC'D + A'BCD' + ABC'D' + ABCD$$

$$= B'(A \text{ xor } C) + A'B(C \text{ xor } D) + AB(C \text{ xnor } D)$$

$$= B'(A \text{ xor } C) + B(A \text{ xor } B \text{ xor } C)$$

1's on diagonal suggest XOR!
Y K-Map not minimal as drawn

gate count
reduced if
XOR available

问题:

如果输入
位宽越来越宽? 是
否仍然使
用卡诺图
进行优化?

答案: **NO**


n-bit 加法器

- Design an n-bit binary adder which performs the addition of two n-bit binary numbers and generates a n-bit sum and a carry out.

- Example: Let n=4

C_{out}	C_3	C_2	C_1	C_0	
	A_3	A_2	A_1	A_0	1 1 0 1 0
+	B_3	B_2	B_1	B_0	+1 1 0 1

	S_3	S_2	S_1	S_0	1 0 1 0

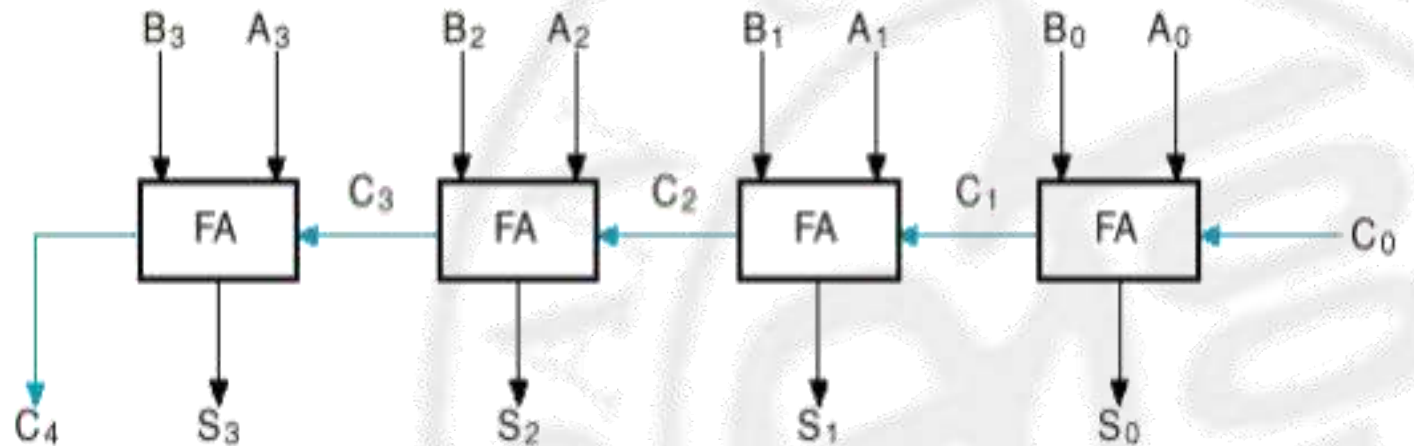

- 存在一种单元电路，可以通过这种电路的级联来完成n-bit加法器

全加器

- 真值表 --> 卡诺图

- C_{i+1} :

$B_i C_i$		A_i	
0	0	1	0
0	0	1	0
0	1	1	1
1	0	1	0
1	1	1	1

- S_i :

$B_i C_i$		A_i	
0	1	0	1
0	1	0	1
1	0	1	0
1	0	1	0
1	1	1	0

A_i	B_i	C_i	S_i	C_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Boolean equations:

- $C_{i+1} = A_i B_i + A_i C_i + B_i C_i$

- $S_i = A_i B_i' C_i' + A_i' B_i' C_i + A_i' B_i C_i' + A_i B_i C_i$
 $= A_i \oplus B_i \oplus C_i$

